

TOTAL: _____/20

ECE 548: Electronic Design I

Homework #3

Due: Friday, March 29th, 2019 (11pm)

Student Name: Thomas Collins

Note:

- Please use this sheet as a cover page.
- Your work must be hand-written (no typing please).
- Homework must be submitted electronically through Canvas in a PDF format.

Do the following problems from Microelectronic Circuit Design by Jaeger & Blalock (5th Edition)

(Pages 137 – 142)

Solve at least 5 of the following list of problems:

3.58, 3.59, 3.63, 3.68, 3.76, 3.89, 3.92, 3.106

(Note: the Q-point refers to the 'operating point' where the load line meets the diode equation.)

ECE 548 Homework #3

3.58, 3.63, 3.76, 3.92, 3.106

Prob # 3.58

A diode has $I_s = 0.1 \text{ fA}$ and is operating at $T = 300 \text{ K}$ (a) What are the values of V_{D0} and r_{D0} if $I_D = 200 \mu\text{A}$?

$$V_T = \frac{kT}{q}$$

$$V_T = \frac{(1.38 \times 10^{-23})(300 \text{ K})}{(1.602 \times 10^{-19} \text{ C})}$$

$$V_T = 0.0258 \text{ V}$$

$$V_D = V_T \ln(1 + I_D / I_s)$$

$$V_D = (0.0258 \text{ V}) \ln(1 + (200 \mu\text{A}) / (0.1 \text{ fA}))$$

$$V_D = 0.732 \text{ V}$$

$$r_{D0} = V_T / I_D$$

$$r_{D0} = (0.0258 \text{ V}) / (200 \mu\text{A})$$

$$V_{D0} = V_D - V_T$$

$$V_{D0} = (0.732 \text{ V} - 0.0258 \text{ V})$$

$$r_{D0} = 129 \Omega$$

$$V_{D0} = 0.7062 \text{ V}$$

(b) If $I_D = 2.0 \text{ mA}$

$$V_D = (0.0258 \text{ V}) (1 + (2.0 \text{ mA}) / (0.1 \text{ fA}))$$

$$V_D = 0.790 \text{ V}$$

$$r_{D0} = (0.0258 \text{ V}) / (2.0 \text{ mA})$$

$$V_{D0} = (0.790 \text{ V} - 0.0258 \text{ V})$$

$$r_{D0} = 12.9 \Omega$$

$$V_{D0} = 0.764 \text{ V}$$

(c) If $I_D = 20 \text{ mA}$

$$V_D = (0.0258 \text{ V}) (1 + (20 \text{ mA}) / (0.1 \text{ fA})) \quad r_{D0} = (0.0258 \text{ V}) / (20 \text{ mA})$$

$$V_D = 0.852 \text{ V}$$


$$r_{D0} = 1.29 \Omega$$

$$V_{D0} = (0.852 \text{ V} - 0.0258 \text{ V})$$

$$V_{D0} = 0.8262 \text{ V}$$

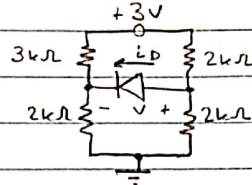
Problem # 3.63

Find the Q point for the circuit in Fig P3.63 using



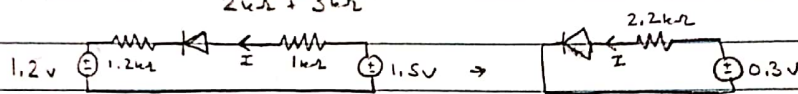(a) the ideal diode model


$$V_{TH} = 3V \left(\frac{2k\Omega}{2k\Omega + 3k\Omega} \right) \quad V_{TH} = 1.2V$$




$$I = 0.3V / 2.2k\Omega \quad I = 0.136mA$$

$$Q_{point} = 0.136mA, 0V$$

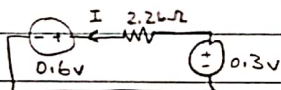(b) The constant voltage drop model with $V_{on} = 0.6V$


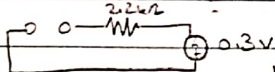
$$I = (0.3V - 0.6V) / (2.2k\Omega) \quad I = -0.136mA$$



$$Q_{point} = 0A, 0.3V$$

(c) Discuss the results.

The constant voltage drop model is the most realistic model because diodes usually only activate around 0.6V.


(d) Use iterative analysis to find the actual Q point. $I_s = 0.1fA$

$$I_D = I_s \left(\frac{V_D}{V_{TH}} \right)$$

$$I_D = (0.1fA) \left(\frac{0.3V}{25mV} \right)$$

$$I_D = 0$$

Problem # 3.76

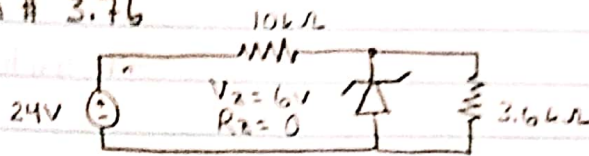

(a) Find the Qpoint for the Zener Diode

$$R_{TH} = 10k\Omega \parallel 3.6k\Omega$$

$$R_{TH} = \frac{10k\Omega \times 3.6k\Omega}{10k\Omega + 3.6k\Omega}$$

$$R_{TH} = 2.65k\Omega$$

$$V_{TH} = 24V \left(\frac{3.6k\Omega}{10k\Omega + 3.6k\Omega} \right)$$

$$V_{TH} = 6.35V$$

$$I = \frac{V_{TH} - V_Z}{R_{TH}}$$

$$I = \frac{6.35V - 6V}{2.65k\Omega}$$

$$I = 0.132mA$$

$$Q_{point} = 0.132mA, 6V$$

(b) Repeat if $R_Z = 100\Omega$

$$R_{TH} = R_{TH}(a) + 100\Omega$$

$$R_{TH} = 2.75k\Omega$$

$$I = \frac{V_{TH} - V_Z}{R_{TH}}$$

$$I = \frac{6.35V - 6V}{2.75k\Omega}$$

$$I = 0.127mA$$

$$Q_{point} = 0.127mA, 6V$$

Prob # 3.92

3.3v 30A DC ripple < 1.5% half wave rec. 60Hz w/ Cap filter

(a) What is the size of the Cap filter?

$$(0.015)(V_r) = \left(\frac{V_p - V_{on}}{R} \right) \left(\frac{T}{C} \right)$$

$$C = \left(\frac{V_p - V_{on}}{R} \right) \left(\frac{T}{0.015 V_r} \right)$$

$$C = (I_p) \left(\frac{1}{f} \right) \left(\frac{1}{0.015 V_r} \right)$$

$$C = (30A) \left(\frac{1}{60\text{Hz}} \right) \left(\frac{1}{(0.015)(3.3v)} \right)$$

$$\boxed{C = 10.1 \text{ F}}$$

(b) What is the PIV rating?

$$\text{PIV} = 2V_p$$

$$= 2(V_{oc} + V_{on})$$

$$= 2(3.3v + 1)$$

w/ Assume $V_{on} = 1v$

$$\boxed{\text{PIV} = 8.6v}$$

(c) What is the r_{ms} value of the trans voltage needed for the rec.

$$V_{rms} = V_p / \sqrt{2}$$

$$V_{rms} = (V_{dc} + V_{on}) / \sqrt{2}$$

$$V_{rms} = (3.3v + 1v) / \sqrt{2}$$

$$\boxed{V_{rms} = 3.041v}$$

(d) What is the value of the peak repetitive diode current in diode.

$$\Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r(0.015)}{V_p}}$$

$$\Delta T = \frac{1}{2\pi(60\text{Hz})} \sqrt{\frac{2(3.3v)(0.015v)}{(3.3v + 1v)}}$$

$$\Delta T = 0.402\text{ms}$$

$$I_p = I_{dc} \frac{T}{\Delta T} \quad I_p = I_{dc} (1/f / \Delta T)$$

$$I_p = (30A) (1/60 / (0.402\text{ms}))$$

$$\boxed{I_p = 1243.78A}$$

(e) what is the surge current at $t = 0^+$?

$$I_{surge} = \omega C V_p$$


$$I_{surge} = (2\pi(60\text{Hz}))(10.1F)(3.3v + 1)$$

$$\boxed{I_{surge} = 16,372.72\text{mA} \sim 16.373A}$$

Prob # 3.106

Repeat Prob # 3.92 for a full wave bridge rectifier.

(a)

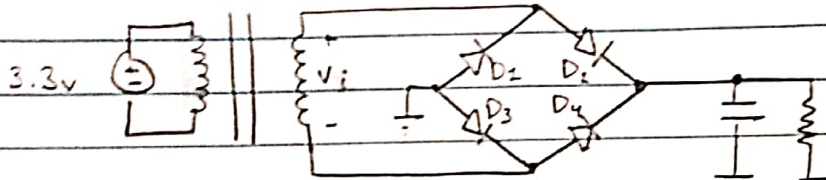

$$V_r = (V_p - V_{on}) \left(\frac{T}{2RC} \right) \quad \text{vs} \quad V_r = (V_p - V_{on}) \left(\frac{T}{RC} \right)$$

$$2C_{full} = V_{half} \quad \boxed{C = 5.05F}$$

(b) PIV

$$PIV = V_p \quad PIV = (V_{dc} + 2V_{on})$$

$$PIV = (3.3V + 2(1V)) \quad \boxed{PIV = 5.3V}$$

(c) V_{rms}

$$V_{rms} = \frac{V_p}{\sqrt{2}} \quad V_{rms} = \frac{(V_{dc} + 2V_{on})}{\sqrt{2}}$$

$$V_{rms} = \frac{(3.3V + 2(1V))}{\sqrt{2}} \quad \boxed{V_{rms} = 3.75V}$$

$$(d) \Delta T = \frac{1}{\omega} \sqrt{\frac{2V_r(0.015)}{V_p}}$$

$$\Delta T = \frac{1}{2\pi(60Hz)} \sqrt{\frac{2(3.3V)(0.015)}{(3.3V + 2(1V))}}$$

$$\boxed{\Delta T = 0.1363ms}$$

$$(e) I_p = I_{dc} \left(\frac{T}{\Delta T} \right)$$

$$I_p = (30A) \left(\frac{1/60Hz}{0.1363ms} \right)$$

$$\boxed{I_p = 1377.41A}$$

[For questions and Further details see solution to problem # 3.92]