

TOTAL: ____/20

ECE 5548: Electronic Design I

Homework #2

Due: Wednesday, February 27th, 2019 (11pm)

Student Name: Thomas Collins

Note:

- Please use this sheet as a cover page.
- Your work must be hand-written (no typing please).
- Homework must be submitted electronically through Canvas in a PDF format.


Do the following problems from Nilsson & Riedel (11th edition)

(Pages 565 – 568)

1. Low-pass filter: Solve at least two of the following problems: 14.1, 14.4, 14.7, 14.8
2. High-pass filter: Solve at least two of the following problems: 14.11, 14.13, 14.15, 14.16
3. Band-pass filter: Solve at least two of the following problems: 14.20, 14.21, 14.24, 14.30

ECE 548 Homework #2

Prob #14.1

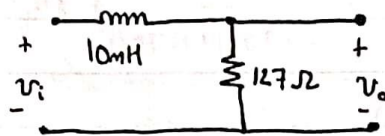

(a) Find the cutoff frequency in hertz for the R-L circuit filter.

$$\omega_c = R/L$$

$$\omega_c = 127 / (10 \times 10^{-3}) \quad \omega_c = 12700 \text{ rad/s}$$

$$12700 \text{ rad/s} \cdot \frac{1}{2\pi} =$$

$$\boxed{\omega_c = 2021.27 \text{ Hz}}$$

(b) Calculate $H(j\omega)$ at ω_c , $0.2\omega_c$, $5\omega_c$

$$H(j\omega) = \frac{R/L}{j\omega + R/L}$$

$$H(j\omega_c) = \frac{R/L}{j\omega_c + R/L}$$

$$H(j\omega_c) = \frac{127\Omega / (10 \times 10^{-3} \text{ H})}{j(12700 \text{ rad/s}) + (127\Omega / (10 \times 10^{-3} \text{ H}))}$$

$$H(j\omega_c) = \frac{12700}{j12700 + 12700} \quad H(j\omega_c) = 0.707 \angle -45^\circ$$

$$\boxed{H(j\omega_c) = 0.707 \angle -45^\circ}$$

$$H(j(0.2\omega_c)) = \frac{12700}{j(0.2)(12700) + 12700}$$

$$H(j(0.2\omega_c)) = \frac{12700}{j2540 + 12700}$$

$$\boxed{H(j(0.2\omega_c)) = 0.981 \angle -11.31^\circ}$$

$$H(j(5\omega_c)) = \frac{12700}{j(5)(12700) + 12700}$$

$$H(j(5\omega_c)) = \frac{12700}{j63500 + 12700}$$

$$\boxed{H(j(5\omega_c)) = 0.196 \angle -78.90^\circ}$$

(c) If $v_i = 10 \cos(\omega t)$ V, write the steady state expression for v_o when $\omega = \omega_c$, $\omega = 0.2\omega_c$, $\omega = 5\omega_c$

$$\omega = \omega_c = 12700$$

$$v_i = 10 \cos(12700 t) \text{ V}$$

$$v_i = 10 \angle 0^\circ$$

$$V_o(j\omega_c) = \frac{R/L}{j\omega_c + R/L} V_i$$

$$V_o(j\omega_c) = \frac{12700}{12700j + 12700} (10 \angle 0^\circ)$$

$$V_o(j\omega_c) = (7.07 \angle -45^\circ) (10 \angle 0^\circ)$$

$$V_o(j\omega_c) = 7.07 \angle -45^\circ$$

$$V_o(j\omega_c) = 7.07 \cos(12700t - 45^\circ) V$$

$$\omega = 0.2\omega_c = 2540$$

$$V_i = 10 \cos(2540t) V$$

$$V_i = 10 \angle 0^\circ$$

$$V_o(j(0.2\omega_c)) = \left(\frac{12700}{2540j + 12700} \right) (10 \angle 0^\circ)$$

$$V_o(j(0.2\omega_c)) = (0.981 \angle -11.31^\circ) (10 \angle 0^\circ)$$

$$V_o(j(0.2\omega_c)) = 9.81 \angle -11.31^\circ$$

$$V_o(j(0.2\omega_c)) = 9.81 \cos(2540t - 11.31^\circ)$$

$$\omega = 5\omega_c = 63500$$

$$V_i = 10 \cos(63500t) V$$

$$V_i = 10 \angle 0^\circ$$


$$V_o(j(5\omega_c)) = \left(\frac{12700}{63500j + 12700} \right) (10 \angle 0^\circ)$$

$$V_o(j(5\omega_c)) = (0.196 \angle -78.90^\circ) (10 \angle 0^\circ)$$

$$V_o(j(5\omega_c)) = 1.96 \angle -78.90^\circ$$

$$V_o(j(5\omega_c)) = 1.96 \cos(63500t - 78.90^\circ)$$

Problem # 14.7

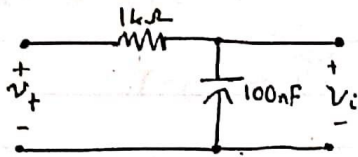

- (a) Find the cutoff frequency (in hertz) of the low pass filter

$$\omega_c = 1/RC = 1/[(1 \times 10^3)(100 \times 10^{-9})]$$

$$\omega_c = 10,000 \text{ rad/s}$$

$$10,000 \cdot \frac{1}{2\pi} = 1591.55 \text{ Hz}$$

$$\boxed{\omega_c = 1591.55 \text{ Hz}}$$

- (b) Calculate $H(j\omega)$ at $\omega_c = \omega_c, \omega_c \cdot (0.1), \omega_c \cdot (10)$

$$H(j\omega_c) = \frac{1/RC}{j\omega_c + 1/RC} = \frac{10000}{10000j + 10000}$$

$$\boxed{H(j\omega_c) = 0.707 \angle -45^\circ} \quad [\text{Same process as prob \# 14.1}]$$

$$H(j0.1\omega_c) = \frac{1/RC}{0.1\omega_c + 1/RC} = \frac{10000}{j1000 + 10000}$$

$$\boxed{H(j(0.1\omega_c)) = 0.995 \angle -5.71^\circ}$$

$$H(j\omega_c(10)) = \frac{1/RC}{10\omega_c + 1/RC} = \frac{10000}{100000j + 10000}$$

$$\boxed{H(j(10\omega_c)) = 0.0999 \angle -84.29^\circ}$$

- (c) If $v_i = 200 \cos(10000t) \text{ mV}$, write the steady state expression for v_o when $\omega = \omega_c, 0.1\omega_c, 10\omega_c$

$$v_i(\omega_c) = 200 \cos(10000t) \text{ mV}$$

$$v_i(\omega_c) = 200 \angle 0^\circ$$

$$v_o(j\omega_c) = \frac{1/RC}{j\omega_c + 1/RC} v_i = \frac{10000}{10000j + 10000} (200 \angle 0^\circ)$$

$$v_o(j\omega_c) = (0.707 \angle -45^\circ) (200 \angle 0^\circ)$$

$$v_o(j\omega_c) = 141.4 \angle -45^\circ$$

$$\boxed{v_o(j\omega_c) = 141.4 \cos(10000t - 45^\circ) \text{ mV}}$$

$$V_i(0.1\omega_c) = 200 \cos(1000t) \text{ mV}$$

$$V_i(0.1\omega_c) = 200 \angle 0^\circ$$

$$V_o(0.1\omega_c \cdot j) = \frac{1/R_C}{0.1\omega_c j + 1/R_C} V_i = \frac{10000}{1000j + 1000} (200 \angle 0^\circ)$$

$$V_o(0.1\omega_c \cdot j) = (0.995 \angle -5.71^\circ) (200 \angle 0^\circ)$$

$$V_o(0.1\omega_c \cdot j) = 199 \cos(1000t - 5.71^\circ) \text{ mV}$$

$$V_i(10\omega_c) = 200 \cos(100000t) \text{ mV}$$

$$V_i(10\omega_c) = 200 \angle 0^\circ$$


$$V_o(10\omega_c) = \frac{1/R_C}{10\omega_c j + 1/R_C} V_i = \frac{10000}{100000j + 1000} (200 \angle 0^\circ)$$

$$V_o(10\omega_c) = (0.0999 \angle -84.29^\circ) (200 \angle 0^\circ)$$

$$V_o(10\omega_c) = 19.98 \angle -84.29^\circ$$

$$V_o(10\omega_c) = 19.98 \cos(100000t - 84.29^\circ) \text{ mV}$$

Problem # 14.11

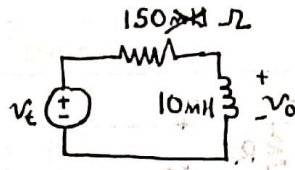

(a) What is the transfer function $H(s) = V_o(s) / V_i(s)$ of this filter

$$V_o = \left(\frac{sL}{sL + R} \right) V_i = \left(\frac{s(10 \times 10^{-3})}{s(10 \times 10^{-3}) + 150} \right) V_i$$

$$\frac{V_o}{V_i} = \frac{s(10 \times 10^{-3})}{s(10 \times 10^{-3}) + 150}$$

$$\frac{V_o}{V_i} = \frac{s}{s + 15000}$$

$$\omega / \frac{V_o}{V_i} = H(s)$$

$$H(j\omega) = \frac{j\omega}{j\omega + 15000}$$

(b) What is the cut off frequency of this filter?

$$\omega_c = \frac{R}{L}$$

$$\omega_c = \frac{150 \Omega}{(10 \times 10^{-3}) \text{ H}}$$

$$\omega_c = 15000 \text{ rad/s}$$

$$\omega_c = 2387.32 \text{ Hz}$$


(c) What is the magnitude of the filter's transfer function at

$$s = j\omega_c$$

$$H(j\omega_c) = \frac{j\omega_c}{j\omega_c + 15000} = \frac{15000}{j15000 + 15000}$$

$$|H(j\omega_c)| = 0.707$$

Problem # 14.16

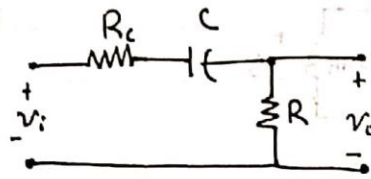

(a) Derive the expression for $H(s)$ where $H(s) = V_o / V_i$

$$V_o(s) = \frac{R}{R_c + R + 1/sC} V_i(s) \Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{R}{R_c + R + 1/sC}$$

$$H(s) = \frac{sRC}{sC(R_c + R) + 1}$$

(b) At what frequency will the magnitude of $H(j\omega)$ be a max.

$$H(j\omega) = \frac{j\omega RC}{j\omega C(R_c + R) + 1} \Rightarrow \frac{RC}{C(R_c + R) + \frac{1}{j\omega}}$$

$$H(j(0)) = \frac{RC}{C(R_c + R) + \frac{1}{j(0)}} \quad H(j(\infty)) = \frac{RC}{C(R_c + R) + \frac{1}{j(\infty)}}$$

$|H(j\omega)|$ is a max at $\omega = \infty$

(c) What is the maximum value of $H(j\omega)$

$$H(j\omega) \rightarrow H(j(\infty)) = \frac{RC}{C(R_c + R)}$$

$$H(j(\infty)) = \frac{RC}{C(R_c + R) + \frac{1}{j(\infty)}} \quad H(j(\infty)) = \frac{RC}{C(R_c + R)}$$

$$H(j(\infty)) = \frac{R}{R_c + R}$$

(d) At what frequency will the magnitude of $H(j\omega)$ equal its maximum divided by $\sqrt{2}$

$$|H(j\omega_c)| = \frac{|H(j\omega)|_{\max}}{\sqrt{2}} \Rightarrow \left| \frac{j\omega_c RC}{j\omega_c C(R_c + R) + 1} \right| = \frac{\frac{RC}{C(R_c + R)}}{\sqrt{2}}$$

$$\frac{\sqrt{(j\omega_c RC)^2}}{\sqrt{(j\omega_c C(R_c + R) + 1)^2}} = \frac{RC}{\sqrt{2} C(R_c + R)}$$

$$(\omega_c RC)^2 = \left(\frac{RC}{\sqrt{2} C(R_c + R)} \right)^2 \left(\sqrt{(j\omega_c C(R_c + R) + 1)^2} \right)^2$$

Problem #14.16 (cont.)

$$\omega_c^2 R^2 C^2 = \frac{R^2 C^2}{2C^2(R_c + R)^2 ((\omega_c C(R_c + R))^2 + 1)}$$

$$\omega_c^2 = \frac{((\omega_c C(R_c + R))^2 + 1)}{2C^2(R_c + R)^2}$$

$$2C^2(R_c + R)^2 \omega_c^2 = (\omega_c C(R_c + R))^2 + 1$$

$$2C^2(R_c + R)^2 \omega_c^2 = \omega_c^2 C^2(R_c + R)^2 + 1$$

$$C^2(R_c + R)^2 \omega_c^2 = 1$$

$$\omega_c^2 = \frac{1}{C^2(R_c + R)^2}$$

$$\boxed{\omega_c = \frac{1}{C(R_c + R)}}$$

(e) Assume a resistance of $12.5k\Omega$ is connected in series with a $5nF$ cap. in the circuit. Calculate ω_c , $H(j\omega_c)$, $H(j(0.2)\omega_c)$ and $H(j(5)\omega_c)$

$$\omega_c = \frac{1}{(5 \times 10^{-9})(12.5k\Omega + 7.5k\Omega)}$$

$$\omega_c = 10000$$

$$H(j\omega_c) = \frac{j\omega_c RC}{j\omega_c C(R_c + R) + 1}$$

$$H(j\omega_c) = \frac{10000j(12.5k)(5nF)}{10000j(5nF)(20k\Omega) + 1}$$

$$H(j\omega_c) = \frac{0.625j}{1 + 1j}$$

$$\boxed{H(j\omega_c) = 0.442 \angle 45^\circ}$$

@ $\omega_c = 10000 \text{ rad/s}$

$$0.2\omega_c = 2000$$

$$H(j(0.2)\omega_c) = \frac{(0.2)j\omega_c RC}{(0.2)j\omega_c C(R_c + R) + 1}$$

$$H(j(0.2)\omega_c) = \frac{2000j(12.5k\Omega)(5nF)}{(2000j)(5nF)(20k\Omega) + 1}$$

$$H(j(0.2)\omega_c) = \frac{0.125j}{0.2j + 1}$$

$$\boxed{H(j\omega_c(0.2)) = 0.123 \angle 11.31^\circ}$$

$$5\omega_c = 50000$$

$$H(5\omega_c j) = \frac{50000j(12.5k\Omega)(5nF)}{(50000j)(5nF)(20k\Omega) + 1}$$

$$H(5\omega_c j) = \frac{3.125j}{5j + 1}$$

$$\boxed{H(5\omega_c j) = 0.613 \angle 78.69^\circ}$$

Problem #14.20

Calculate the center frequency, the bandwidth and the quality factor of a bandpass filter that has an upper cutoff frequency of 121 krad/s and a lower cutoff frequency of 100 krad/s .


$$\begin{aligned}\omega_0 &= \sqrt{\omega_{c1} \cdot \omega_{c2}} \\ &= \sqrt{(121 \text{ krad/s})(100 \text{ krad/s})} \\ \omega_0 &= 110 \text{ krad/s}\end{aligned}$$

$$\begin{aligned}\beta &= \omega_{c1} - \omega_{c2} \\ \beta &= 121 \text{ krad/s} - 100 \text{ krad/s} \\ \beta &= 21 \text{ krad/s}\end{aligned}$$

$$Q = \omega_0 / \beta = \frac{110 \text{ krad/s}}{21 \text{ krad/s}}$$

$$Q = 5.238$$

Problem #14.24

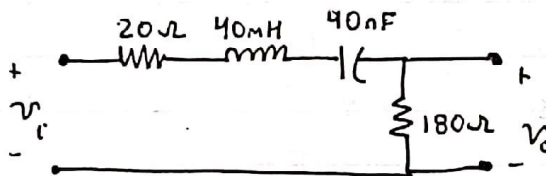

$$(a) f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(40 \text{ mH})(40 \text{ nF})}} \quad f_0 = 3978.87 \text{ Hz}$$

$$(b) Q = \frac{\sqrt{L/C}}{R+R_1} = \frac{\sqrt{\frac{40 \text{ mH}}{40 \text{ nF}}}}{20 \Omega + 180 \Omega} \quad Q = 5$$

$$(c) \omega_{c1} = \frac{R+R_1}{2L} + \sqrt{\left(\frac{R+R_1}{2L}\right)^2 + \frac{1}{LC}} = \frac{180 \Omega + 20 \Omega}{2(40 \text{ mH})} + \sqrt{\left(\frac{180 \Omega + 20 \Omega}{2(40 \text{ mH})}\right)^2 + \frac{1}{40 \text{ mH} \cdot 40 \text{ nF}}}$$

$$\omega_{c1} = 22.624 \text{ krad/s}$$

$$f_{c1} = \frac{\omega_{c1}}{2\pi} = \frac{22.624 \text{ krad/s}}{2\pi} \quad f_{c1} = 3.6 \text{ kHz}$$

$$(d) \omega_{c2} = \frac{R+R_1}{2L} + \sqrt{\left(\frac{R+R_1}{2L}\right)^2 + \frac{1}{LC}} = \frac{180 \Omega + 20 \Omega}{2(40 \text{ mH})} + \sqrt{\left(\frac{180 \Omega + 20 \Omega}{2(40 \text{ mH})}\right)^2 + \frac{1}{40 \text{ mH} \cdot 40 \text{ nF}}}$$

$$\omega_{c2} = 27.624 \text{ krad/s} \quad f_{c2} = \frac{\omega_{c2}}{2\pi} = \frac{27.624 \text{ krad/s}}{2\pi} \quad f_{c2} = 4.396 \text{ kHz}$$

$$(e) \beta = \omega_{c2} - \omega_{c1} = 27.624 \text{ krad/s} - 22.624 \text{ krad/s} \quad \beta = 5 \text{ krad/s}$$

$$f_B = \frac{\beta}{2\pi} = \frac{5 \text{ krad/s}}{2\pi} \quad f_B = 796 \text{ Hz}$$