

**TOTAL: \_\_\_\_/20**

**ECE 5548: Electronic Design I**

**Homework #1**

**Due: Monday, February 11<sup>th</sup>, 2019 (11pm)**

**Student Name:** Thomas Collins

**Note:**

- Please use this sheet as a cover page.
- Your work must be hand-written (no typing please).
- Homework must be submitted electronically through Canvas in a PDF format.

**Do the following problems from Nilsson & Riedel (11<sup>th</sup> edition)**

(Page 513)

1. Example 13.12
2. Assessment Problem 13.12

(Page 533)

3. Problem 13.78
4. Problem 13.79
5. Problem 13.80




Thomas Collins

ECE 548

Due 2/11/2018

ECE 548

1. Example 13.12

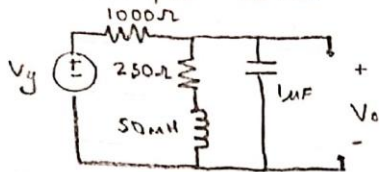

$$v_g = 120 \cos(5000t + 30^\circ) \text{ V}$$

$$Z_1 = 1000 \Omega$$

$$Z_2 = 250 \Omega$$

$$Z_3 = sL = j(5000 \cdot 50 \cdot 10^{-3}) = 0.05s \Omega$$

$$Z_4 = 1/sC = 1/j(5000 \cdot 1 \times 10^{-6}) = 10^6/s \Omega$$

$$\frac{V_o - V_g}{1000} + \frac{V_o}{250 + 0.05s} + \frac{V_o s}{10^6} = 0$$

$$(V_o - V_g)(250 + 0.05s) + V_o + \frac{V_o s (250 + 0.05s)}{10^6} = 0$$

$$(V_o - V_g)(250 + 0.05s)(1000) + (10^6)V_o + V_o s (250 + 0.05s) = 0$$

$$(250V_o + 0.05sV_o - 250V_g - 0.05sV_g)(1000) + (10^6)V_o + 250V_o s + 0.05V_o s^2 = 0$$

$$(2.5 \times 10^5)V_o + 50sV_o - (2.5 \times 10^5)V_g - 50sV_g + (10^6)V_o + 250V_o s + 0.05V_o s^2 = 0$$

$$0.05V_o s^2 + 50sV_o + 250sV_o + (2.5 \times 10^5)V_o + (10^6)V_o - 50sV_g - (2.5 \times 10^5)V_g = 0$$

$$V_o (s^2 \cdot 0.05 + 300s + 1.25 \times 10^6) = (50s + 2.5 \times 10^5)V_g$$

$$V_o = \frac{(50s + 2.5 \times 10^5)V_g}{(s^2 \cdot 0.05 + 300s + 1.25 \times 10^6)} \quad V_o = \frac{1000(s + 5000)V_g}{(s^2 + 6000s + 25 \times 10^6)}$$

$$(s^2 \cdot 0.05 + 300s + 1.25 \times 10^6) \quad (s^2 + 6000s + 25 \times 10^6)$$


$$H(j5000) = \frac{1000(j5000 + 5000)V_g}{(j5000^2 + 6000 \cdot j5000 + 25 \times 10^6)}$$

$$H(j5000) = \frac{1 + j1}{j6} = \frac{1 - j1}{6} = \frac{\sqrt{2}}{6} \angle -45^\circ$$

$$V_{oss} = (120) \frac{\sqrt{2}}{6} \cos(5000t + (30^\circ - 45^\circ))$$

$$V_{oss} = 20\sqrt{2} \cos(5000t - 15^\circ)$$

## 2 Assessment Problem #13.12

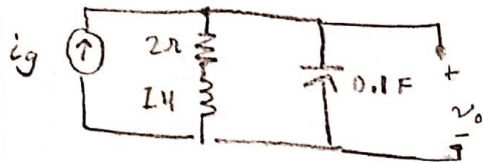

$$i_g = 10 \cos(4t) \text{ A}$$

$$H(s) = \frac{Z_{out}(s)}{I_{in}(s)}$$

$$Z_1 = 2\Omega$$

$$Z_2 = sL = s$$

$$Z_3 = 1/sC = 10/s$$

[How do I get the Transfer func?]

$$H(s) = \frac{10(s+2)}{(s^2 + 2s + 10)}$$

$$H(j4) = \frac{10(j4+2)}{(j4)^2 + 2(j4) + 10} = \frac{20 + 40j}{-16 + 8j + 10} = \frac{20 + 40j}{-6 + 8j}$$

$$\frac{44.72 \angle 63.43^\circ}{7.21 \angle 33.69^\circ} \quad \text{[Where does the denominator go???.]}$$

$$V_{out} = 44.72 \cos(4t - 63.43^\circ)$$

3. Problem #13.78 prob #13.79 in 10<sup>th</sup>

linear time-invariant circuit

$$H(s) = \frac{I_o}{I_g} = \frac{125(s + 400)}{s(s^2 + 200s + 10^4)}$$

If  $i_g = 80 \cos 500t$  A, what is the steady-state expression for  $i_o$

$$H(j\omega) = \frac{125(j\omega + 400)}{(j\omega)((j\omega)^2 + 200(j\omega) + 10^4)}$$

$$= \frac{125(j\omega + 400)}{j\omega(-\omega^2 + 200j\omega + 10^4)}$$

$$H(j500) = \frac{125((j500) + 400)}{(j(500))((-500^2) + 200(j500) + 10^4)}$$

$$H(j500) = \frac{125(640.31 \angle 51.34^\circ)}{500 \angle 90^\circ (260000 \angle 157.38^\circ)} = \frac{80038.75 \angle 51.34^\circ}{1.3 \times 10^8 \angle 247.38^\circ}$$

$$H(j500) = 6.1568 \times 10^{-4} \angle -196.04^\circ$$

$$i_{out} = (6.1568 \times 10^{-4})(80) \cos(500t - 196.04^\circ) \text{ A}$$

$$i_{out} = (0.049) \cos(500t - 196.04^\circ) \text{ A}$$



4. Problem # 13.79 Altered # 13.78 in 10<sup>th</sup> edition

The transfer function for a linear time-invariant circuit is

$$H(s) = \frac{V_o}{V_g} = \frac{4(s+3)}{s^2 + 8s + 41}$$

$$V_g = 40 \cos(3t) \text{ V}$$

$$H(j\omega) = \frac{4(j\omega + 3)}{(j\omega)^2 + 8j\omega + 41} = \frac{4j\omega + 12}{-\omega^2 + 8j\omega + 41}$$

$$H(3j) = \frac{4j(3) + 12}{-(3j)^2 + 8j(3) + 41} = \frac{12j + 12}{9 + 24j + 41} = \frac{12 + 12j}{50 + 24j}$$

$$\frac{16.97 \angle 45^\circ}{55.46 \angle 25.64^\circ} = 0.306 \angle 19.33^\circ$$

$$V_{out} = (40)(0.306) \cos(3t + 19.33^\circ)$$

$$V_{out} = 12.239 \cos(3t + 19.33^\circ)$$

5 Problem #13.80 Prob #13.80 in 10th edition

When an input voltage of  $30u(t)$  V is applied to a circuit the response is known to be

$$V_o = (50e^{-8000t} - 20e^{-5000t}) u(t) \text{ V}$$

What will the steady state response be if

$$V_g = 120 \cos(6000t) \text{ V}$$

L-T

$$30u(t) \text{ V} = 30/s \text{ V}$$

$$V_o = \left( \frac{50}{(s+8000)} - \frac{20}{(s+5000)} \right) \text{ V}$$

$$H(s) = \left( \frac{50}{(s+8000)} - \frac{20}{(s+5000)} \right) \text{ V} = s \left( \frac{(50s + 250000) - (20s + 100000)}{30(s+8000)(s+5000)} \right)$$

$$= s \left( \frac{\frac{30}{s} (30s + 90000)}{30(s+8000)(s+5000)} \right)$$

$$H(s) = \frac{s(s+3000)}{(s+8000)(s+5000)}$$

$$H(j\omega) = \frac{(j\omega)(j\omega+3000)}{(j\omega+8000)(j\omega+5000)} \Rightarrow \frac{(j6000)(j6000+3000)}{((j6000)+8000)((j6000)+5000)}$$

$$H(j6000) = \frac{-36 + j18}{4 + j75} = \frac{40.249 \angle 153.434^\circ}{78.102 \angle 87.064^\circ}$$

$$H(j6000) = 0.515 \angle 66.37^\circ$$

$$V_{out} = (0.515)(120) \cos(6000t + 66.37^\circ)$$

$$V_{out} = 61.84 \cos(6000t + 66.37^\circ)$$